

Assignment 13: MOSFET as a switch

(Solutions will be provided on 16th Nov.)

1. This problem is concerned with the design of a MOSFET switch which must satisfy a prescribed static discipline. The transistor has the following characteristics:

On resistance: 100 to 500 ohms

Threshold voltage: 1.8 to 2.6 V

(These ranges reflect the normal manufacturing variances for a specific FET type)

The available voltage is 5V. For reasons of switching speed, the resistance R_L between the drain and the power supply may not exceed 10k ohms. The static discipline is:

$$\begin{array}{ll} V_{OH} = 4.5 \text{ V} & V_{IH} = 3 \text{ V} \\ V_{IL} = 1.5 \text{ V} & V_{OL} = 0.5 \text{ V} \end{array}$$

- (a) What are the permissible ranges for R_L that satisfy the static discipline

Sol: We use the switch-resistor model (SR) model:

MOSFET OFF $\Rightarrow V_{out} = 5 \text{ V}$ (ok)

MOSFET ON $\Rightarrow V_{out} = \frac{R_{ON}}{(R_{ON} + R_L)} \times 5 \text{ V}$ which should be at least 0.5 ($=V_{OL}$)

When R_{ON} is small and R_L is large, V_{out} will be small. So the worst case for V_{out} occurs when: R_{ON} is large and R_L is small. Since $R_{ON} < 500$, R_L should be at least 4.5 kohms or else V_{out} could exceed 0.5 V. Upper limit is of course 10k.

- (b) What is the noise margin for a low input

Sol: The usual definition is simply $1.5 - 0.5 = 1 \text{ V}$

Clarification: We can choose R_L according to our needs

However, we cannot choose R_{ON} or V_T . For such problems you must design R_L taking into account the worst possible values of R_{ON} and V_T . Imagine an adversary sitting inside the transistor trying to set the values of these parameter (R_{ON} and V_T) to ruin your day.

However, given the MOSFET specifications, the actual noise margin is higher. So let us choose R_L to be as large as possible (to ensure a small V_{out}). As before, the worst case R_{ON} value is 500 ohms so that V_{out} is at most $= 5 \left(\frac{500}{500 + 10000} \right) = 0.24$ (it will be smaller for larger values of R_{ON} but we cannot be wishful).

From the perspective of choosing R_L , this is the lowest V_{out} (since we want a low V_{out})
From the perspective of transistor, this is the highest V_{out} (the adversary inside the transistor will test all values of R_{ON} will come to this conclusion).

Similarly, a low input is guaranteed as long as $V_{GS} < V_T$, so the MOSFET switch will continue to work so long as the input voltage is less than 1.8 V. (worst value of V_T). Again, it could be higher for higher V_T but we cannot be too optimistic.

Now consider a communication channel: The MOSFET at the transmitter will produce a “low” voltage of 0.24 V in when ON. Add noise to it, and we can still have the MOSFET at the receiver end interpret the received voltage of 1.8 V as “low.” So the noise margin is actually $1.8 - 0.24 = 1.56$ V. Note that such calculations can only be done when V_T , R_L and R_{ON} are given.

(c) What is the noise margin for a high input

Sol: Again, the usual definition is $4.5 - 3 = 1.5$ V. But all input voltages higher than 2.6 V are always interpreted as “high”. Similarly, the MOSFET always provides 5V at the output since R_{OFF} is infinite.

So a “high” voltage of 5V produced at the output can decay all the way up to 2.6 V and still be interpreted as “high” The noise margin is therefore: $5 - 2.6 = 2.4$ V

(d) Assume that n of these transistors are used to create a multiple-input NAND gate. What is the value of R_L that maximizes n ?


Sol: Recall the multi-input NAND gate circuit. Suppose the output is “low” which happens all inputs are “high.” In this case, all the n MOSFETs will be ON, resulting in a series resistance of $n \times R_{ON}$. So we have that $V_{out} = \frac{nR_{ON}}{(nR_{ON} + R_L)} \times 5$ V which should be at most 0.5 V to ensure static discipline. Clearly, we need the largest possible value of R_L to ensure that V_{out} remains below 0.5. So R_L should be 10k.

(e) What is the largest value of n ?


Sol: So let us say that $R_L = 10$ k. Then for the worst case value of R_{ON} , we can only have $n=2$ (in which case $V_{out} = 0.45$ V). Note that a higher value of n may be realizable in practice if R_{ON} can be measured. But as a designer, one must always assume the worst case values.

 2. A three terminal device shown has the characteristics indicated: when v is less than 3V, terminal c is connected to terminal a. When v is greater than 4 V, terminal c is isolated and I must be zero.

- Devise and sketch a circuit in which this device functions as a buffer. Label input and output terminals. Prepare a truth table showing values of the input and output voltages of your circuit



 A buffer is a circuit which gives low for low input and high for a high input. The required circuit is:




The required table is:

V_{in}	V_{out}
0-3 V	0 V
4-5 V	5 V


b. Using one or more of these devices, devise and sketch a two-input AND gate

Sol:

 


c. Repeat for a two-input OR gate

Sol:

 


d. Can you use this device to create an inverter? Explain.

Sol:

 

 3. Consider the n-input NOR gate shown below. Assume that each transistor has an ON resistance of R_{ON} .

- For what set of inputs does the gate consume the maximum amount of power?
- Derive an expression for this worst case power
- What is the value of the worst case power for $R=10k$ and $R_{ON} = 0.5k$, $V_S = 5V$?



Sol:

(a) Here, note that R is part of the gate. Most power is consumed when all gates are ON

(b) Worst case power is given by $V_S^2 / \left(\frac{R_{ON}}{n} + R_L \right)$ since all the MOSFETs will be in parallel. This expression is maximized when n goes to infinity.

(c) Substitute to obtain $0.05n/(20n+1)$ which ranges from 2.43 ($n=2$) to 2.5 (n large) mW