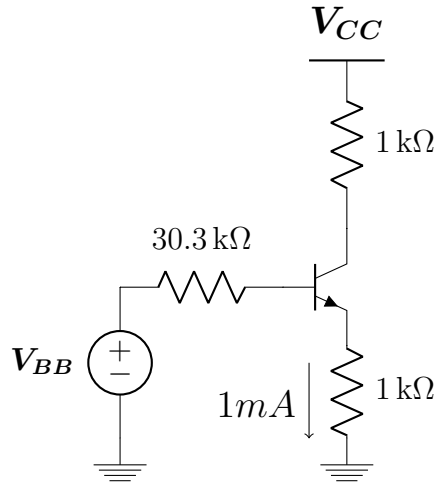


Assignment 8


ESC 201

Basic


1. Determine the value of voltage V_{BB} so that dc emitter current is 1mA. Determine also the minimum supply voltage V_{CC} necessary so that transistor operates in forward active mode. Assume that current gain $\beta_F = 100$.



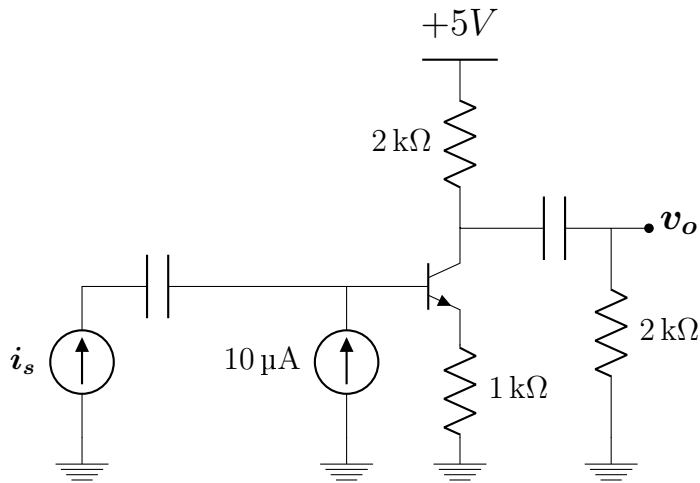
2. For the circuit shown below, carry out ac analysis to determine the ratio $\mathbf{v_o}/\mathbf{i_s}$, where $\mathbf{v_o}$ is ac output voltage and $\mathbf{i_s}$ is ac sinusoidal current. Assume that transistor is biased in forward active mode and current gain $\beta_F = 100$.



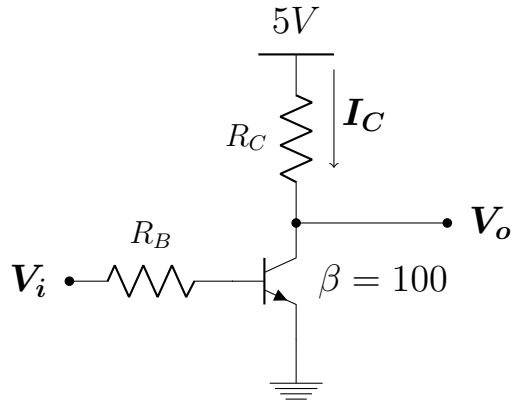3. Determine R_B and R_C such that the transistor is in saturation with $I_C = 2\text{ mA}$ and $\beta_{\text{forced}} = 20$ when $V_i = 5\text{ V}$. Draw the voltage transfer characteristics (a plot of V_o vs V_i) with these resistances.




4. Determine I_C and V_{CE} .

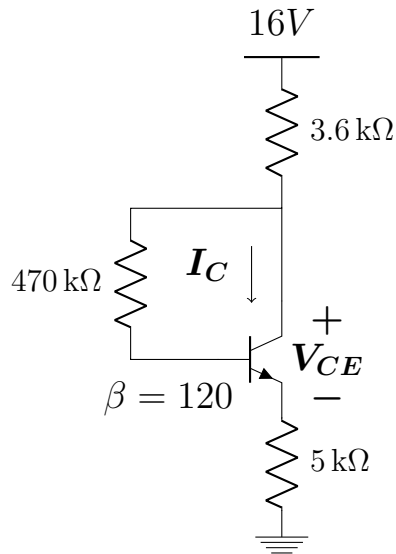


Advanced

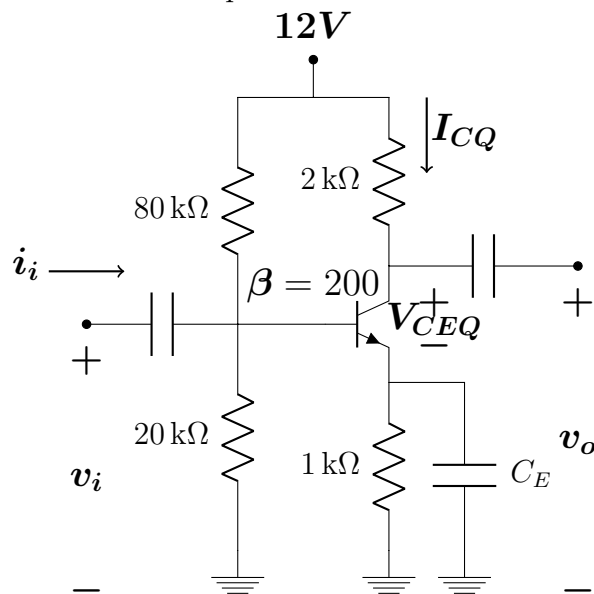5. For the following common emitter amplifier circuit:




- (a) Calculate V_{CEQ} and I_{CQ} .
- (b) Calculate the small signal voltage gain $A_v = \frac{v_o}{v_i}$ and the input impedance $Z_i = \frac{v_i}{i_i}$.
- (c) What will the small signal voltage gain and the input impedance be if C_E is removed from the circuit?


6. Consider the following circuits

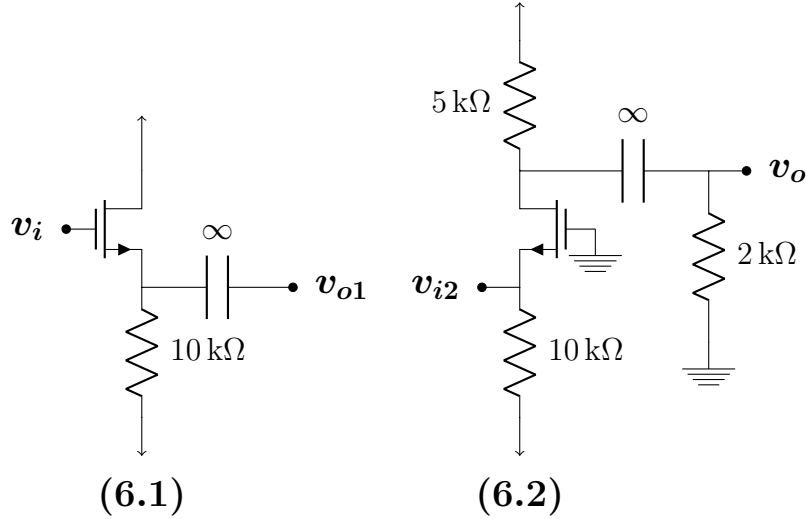

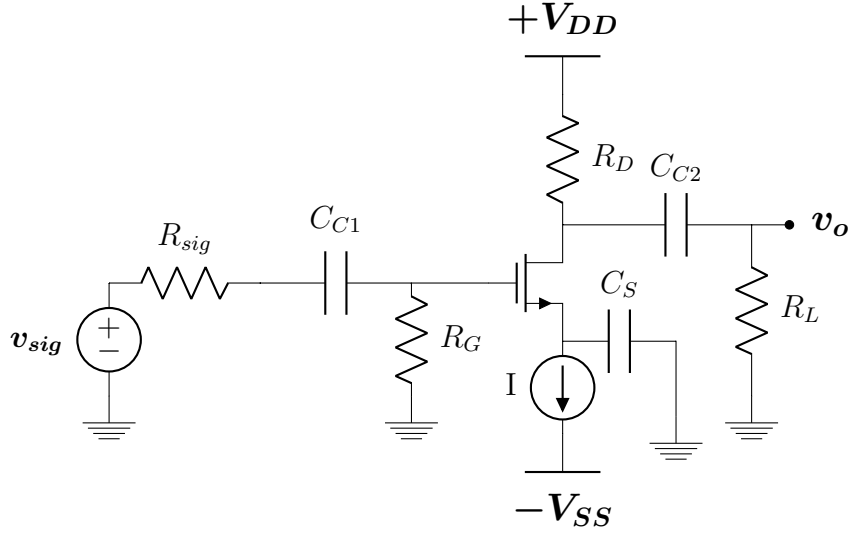- (a) The NMOS transistor in the source follower circuit shown in Fig.(6.1) has $g_m = 5\text{mA/V}$ and a large r_o . Find the open-circuit voltage gain and the output resistance.
 - (b) The NMOS transistor in the common-gate amplifier shown in Fig.(6.2) has $g_m = 5\text{mA/V}$ and a large r_o . Find the input resistance and the voltage gain.
 - (c) If the output of the source follower in Fig.(6.1) is connected to the input of the common-gate amplifier in Fig.(6.2), use the results of (a) and (b) to obtain the overall voltage gain $\frac{v_o}{v_i}$.
7. Calculate the overall voltage gain $G_v = v_o/v_{sig}$ of a common source amplifier, shown in below, which has $g_m = 2\text{mA/V}$, $r_o = 50\text{k}\Omega$, $R_D = 10\text{k}\Omega$, $R_G = 10\text{M}\Omega$. The amplifier is fed from a signal source with a resistance, R_{sig} of $0.5\text{k}\Omega$ and amplifier output is coupled to a load resistance, R_L of $20\text{k}\Omega$.



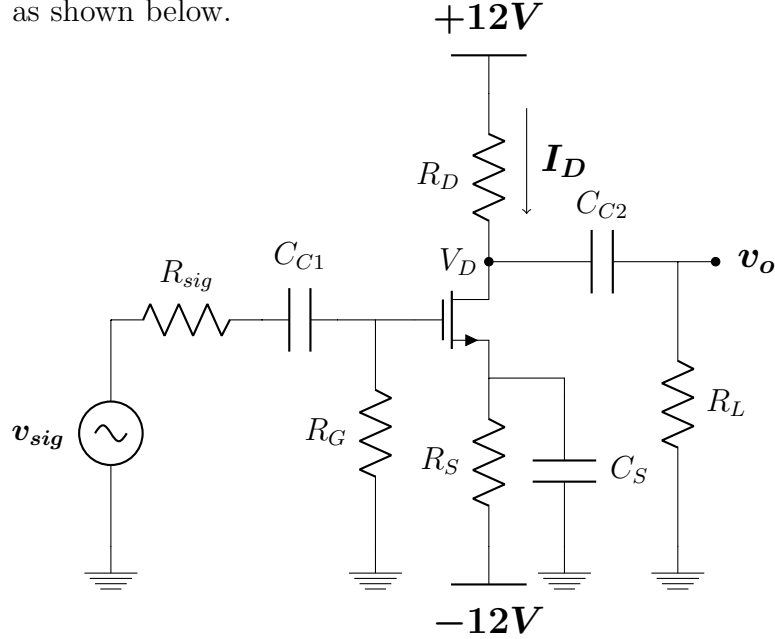8. The common source amplifier is designed using MOSFET [$V_t = 1V$, $k'_n W/L = 0.8 \text{ mA/V}^2$ and $V_A = 50V$] as shown below.



- For the MOSFET to operate in saturation region, it is biased such that drain current $I_D = 0.1 \text{ mA}$ and drain voltage $V_D = 0.5V$. Determine the values of R_D and R_S .
- Determine the values of g_m and r_o at the bias point [$g_m = \frac{2I_D}{V_{GS} - V_t}$, $r_o = \frac{V_A}{I_D}$].
- Given $R_{sig} = 1 \text{ M}\Omega$, $R_G = 9 \text{ M}\Omega$ and $R_L = 85 \text{ k}\Omega$, determine the voltage gain from signal source to load ($G_v = v_o/v_{sig}$).
- What should be the maximum amplitude of input signal v_{sig} so that the MOSFET always operates in saturation region ?
- What happens to the output voltage v_o of the amplifier if amplitude of the input signal v_{sig} is larger than the value calculated in part (d).