

CS220: Lab#7A

1. Implement a register file having 32 registers where each register is 16-bit wide. The register file interface needs to be designed such that it has two read ports and one write port. You need to write an interface module to access the register file. The module should have the following inputs: two read addresses, one write address, one write data, and three bits that specify which of the three ports have valid address inputs. The outputs of the module are the two read data values. Initialize the registers with zero values. Write a top-level module to demonstrate that the register file works. This module defines eight commands to interact with the register file access module. These commands are listed below along with the binary encoding of them in parentheses.

- No read, one write (000)
- One read, no write (001)
- Two reads, no write (010)
- One read, one write (011)
- Two reads, one write (100)
- Two reads, add two read values, write the result (101)
- Two reads, subtract second read value from the first value, write the result (110)
- One read, shift the read value left, write the result (111)

Take the three-bit command as input using slide switches. Depending on the command, your hardware should accept further inputs. For example, if the command is 010, you will have to enter the addresses of two registers also. If the command is 000, you will have to enter the address of a register and the 16-bit data that will be written to the register. If the command is 100, you will have to enter the addresses of two read registers and one write register, and the 16-bit value to be written. If the command is 101, 110, or 111, you will have to enter the addresses of two read registers and one write register. If the command is 111, you also have to enter the shift amount (maximum 15). Use whatever means you know of to accept the inputs. Also, keep a provision of aborting an input midway and starting over. For commands 101, 110, and 111, the writing of the result should be done after the operation completes. Assume that the operation takes 16 cycles. Assume that register read takes two cycles and register write takes two cycles. On execution of each command, the output will have to be shown in the LCD. For each command, the output is defined in the following. Feel free to introduce additional modules.

- If command is 000, the first line of output is the address of the register in binary and the second line of output is the 16-bit value written.
- If command is 001, the first line of output is the address of the register in binary and the second line of output is the 16-bit value read.
- If command is 010, the first line of output is the first 16-bit value read and the second line of output is the second 16-bit value read.
- If command is 011, the first line of output is the address of the register read in binary and the second line of output is the 16-bit value read.

- If command is 100, the first line of output is the first 16-bit value read and the second line of output is the second 16-bit value read.
- If command is 101 or 110 or 111, the first line of output is the address of the register written in binary and the second line of output is the 16-bit value written.

Grading policy: No marks for faulty attempts. Correct implementation of the first five commands will carry 3 marks each. Each of the last three commands will carry 5 marks each. The overall marks will be scaled down by 10 so that the total contribution of this lab is 3 design marks.